


Embedded Systems Hardware (EED-308)



Data Converters

Digital to Analog Converters (DAC)

R-2R Ladder DAC

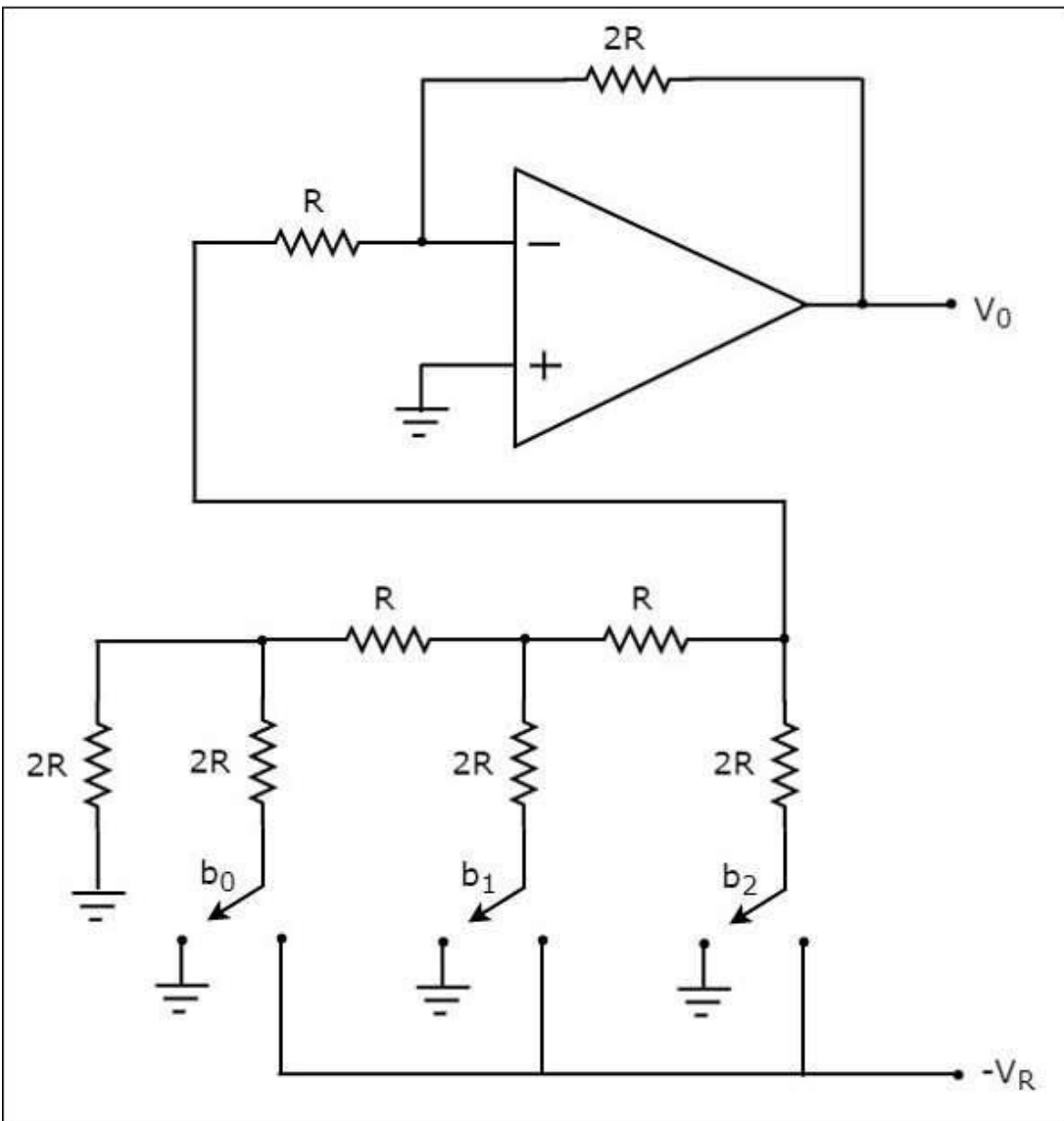

$$V_0 = \frac{V_R}{2} \left\{ \frac{b_{N-1}}{2^0} + \frac{b_{N-2}}{2^1} + \dots + \frac{b_0}{2^{N-1}} \right\}$$

R-2R Ladder DAC

Advantage:

- ✓ Only two resistor values
- ✓ Does not need as precision resistors as Binary weighted DACs
- ✓ Cheap & easy to manufacture
- ✓ Faster response time

Disadvantages

- ✓ Slower conversion rate
- ✓ More confusing analysis

